




# Mansoura University Faculty of Engineering ECE Department.



## EMG Controlled Hand

Supervisor by :

Dr /Ahmed  
Elnakib

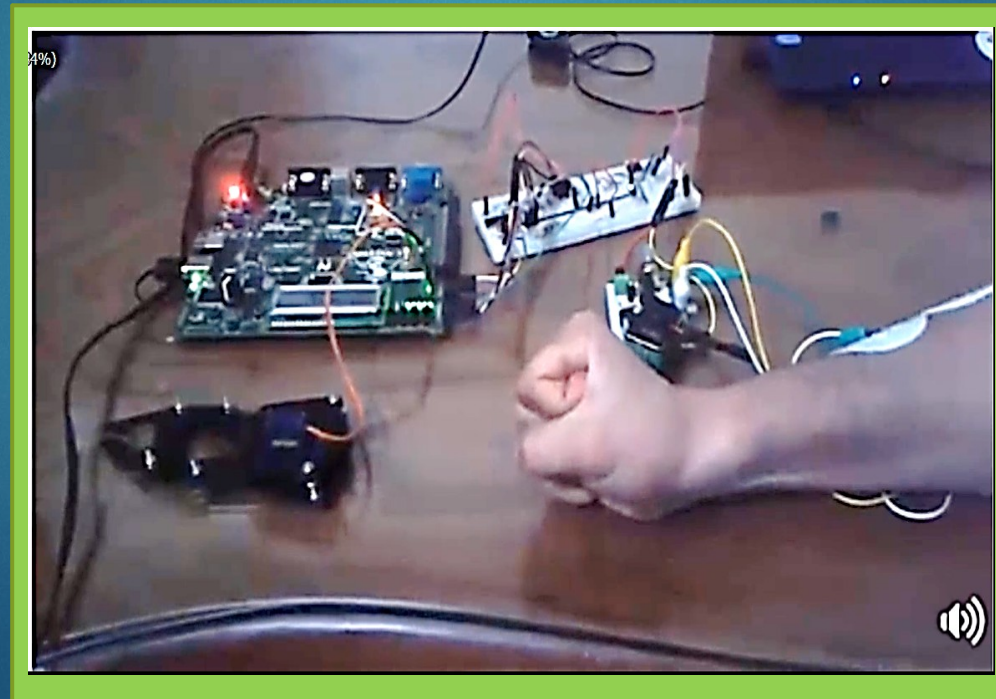

- : Done By
- Ahmed Reda
  - Ehab Abdo
  - Ahmed Omar
  - Mohamed AKL



# ➤ The idea of our project :

- We use the signal of the muscle to control the gripper.

## ➤ The benefit of the project:

- Many people like soldiers lose their hands or any others limbs in war so we can use this project as Prostheses.

# ➤ EMG electrical potential c/cs:


## ➤ Amplitude:

➤ -70 → 30 mv (peak to peak)

## ➤ Frequency Range:


➤ 10 → 450 HZ .

➤ 50 → 150 HZ (dominate energy)

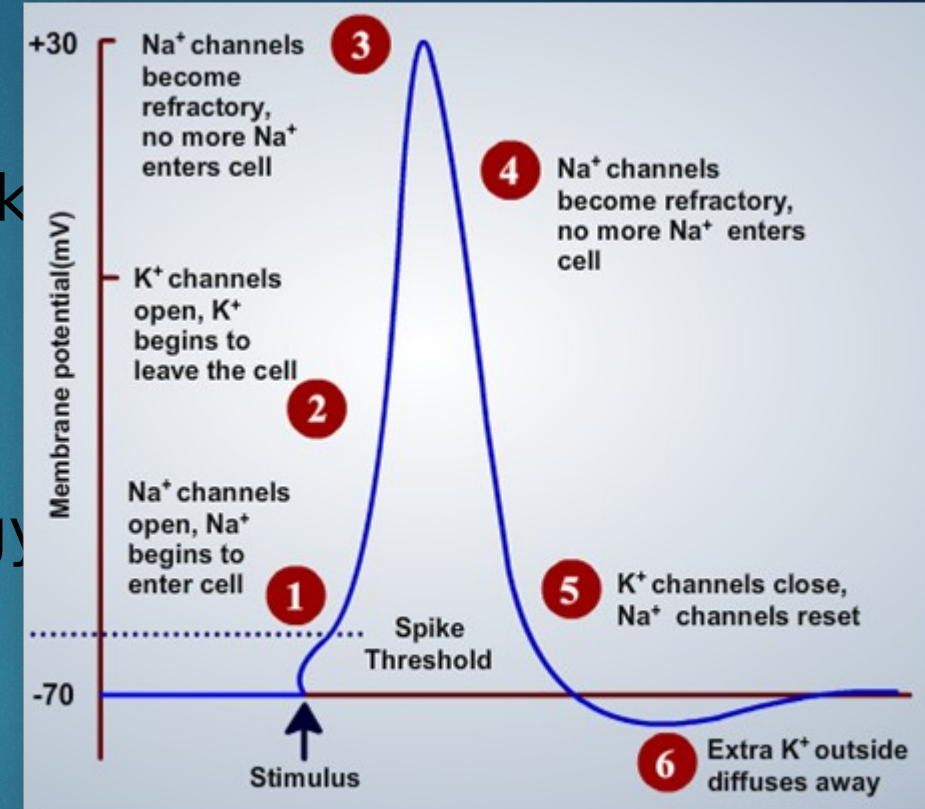



# ➤ Block Diagram:

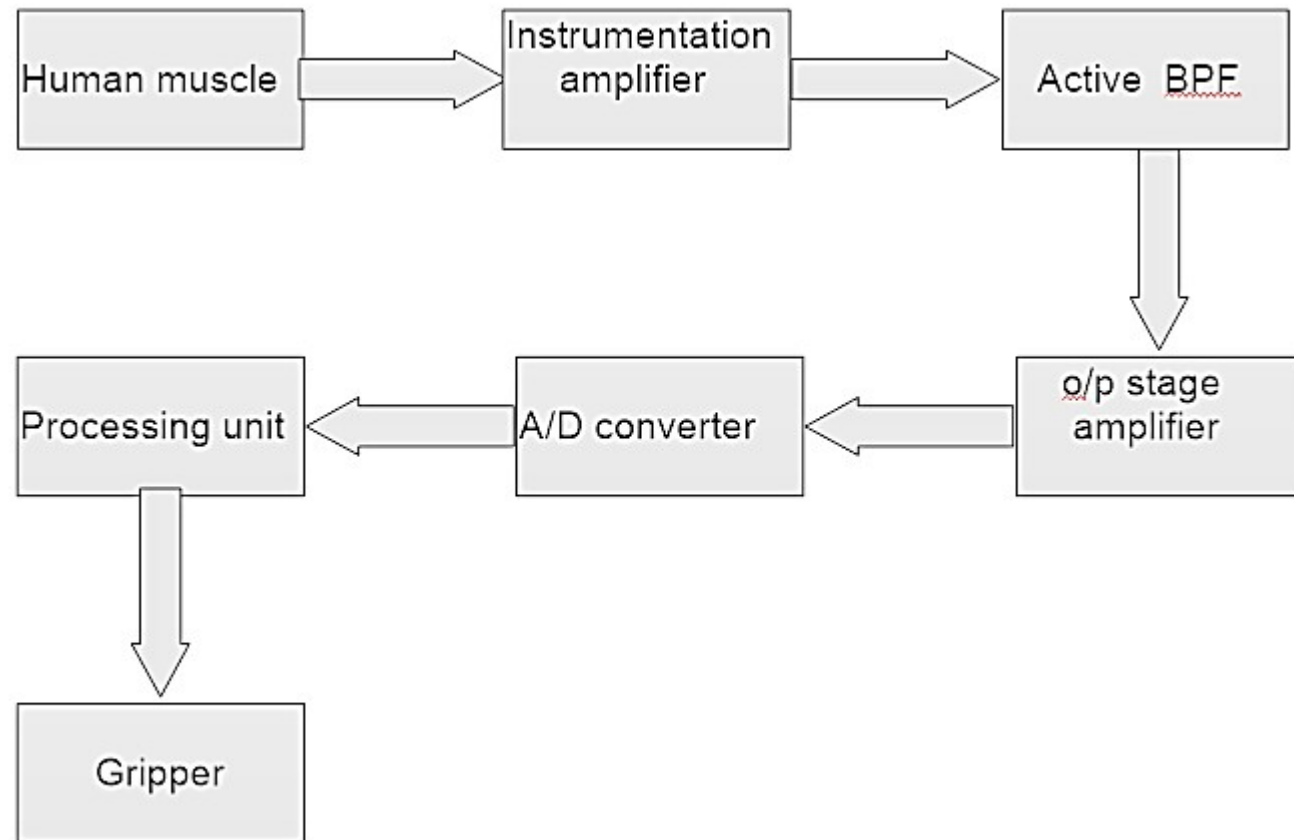

# ➤ Used hardware:

- 1) FPGA.
- 2) Instrumentation amp AD620.
- 3) Gripper.
- 4) 2 \* MC33078.
- 5) 3 \* ECG electrode.
- 6) ADC 0804.



## ➤ ECG electrode:

- We used it instead of EMG electrode because it was cheap and available.
- We used it to read the signal from the hand muscle.
- We used three of it two for positive and negative and one as a reference.
- It is skin surface electrode (non-invasive).





## ➤ Instrumentation amp

### AD620:

- Easy to use.
- Gain set with one external resistor (gain range 0 to 10000)


$$G = (48.4\text{K}\Omega / R_g) + 1.$$

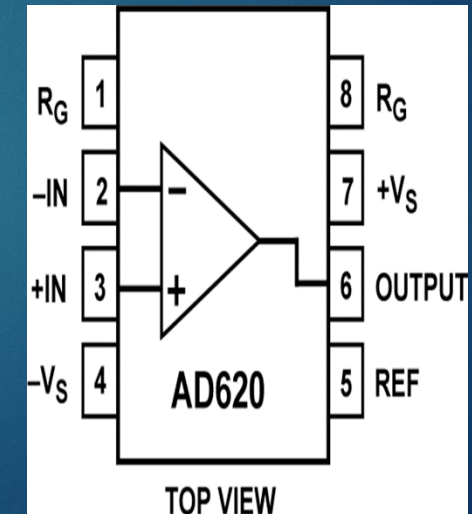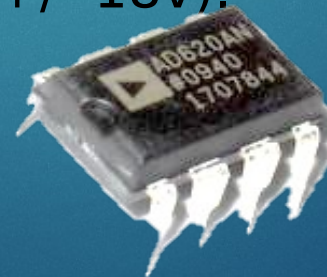- Wide power supply range (+/- 2.3V to +/- 18V).
- 50  $\mu\text{V}$  max input offset voltage.
- Higher performance.
- Excellent dc performance (B grade).



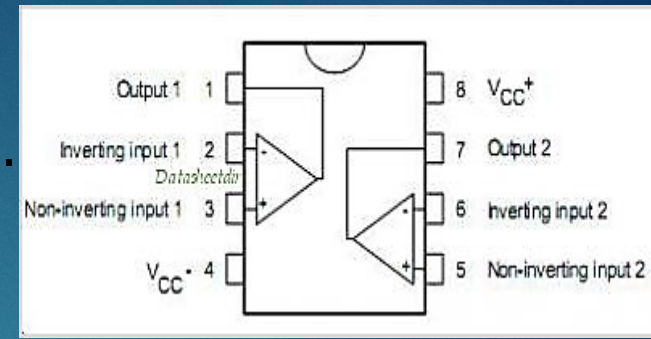
## ➤ Features of MC33078:

- Wide power supply range(+/- 5V to +/- 18v).
- Low noise voltage.
- Low input offset voltage (0.15 mV).



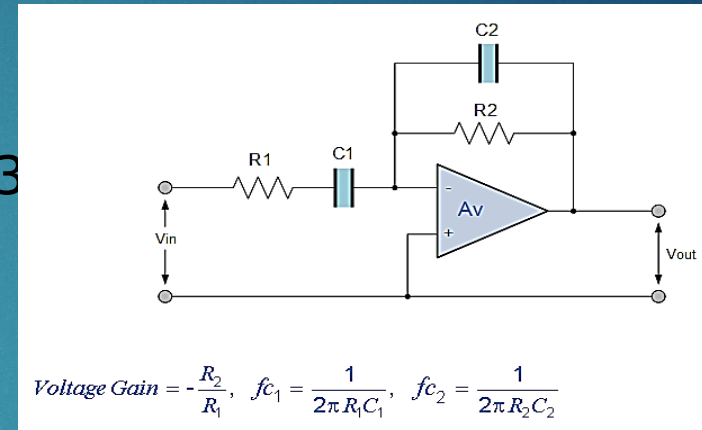
## ➤ BPF using MC33078:

- We used BPF to decrease the noise.
- $R1=1.6k\Omega$  ,  $C1=2\mu f$  ,  $R2=200k\Omega$  ,  $C2=3$
- $F1=50\text{ Hz}$  and  $F2=265\text{ Hz}$  .
- Gain=125.


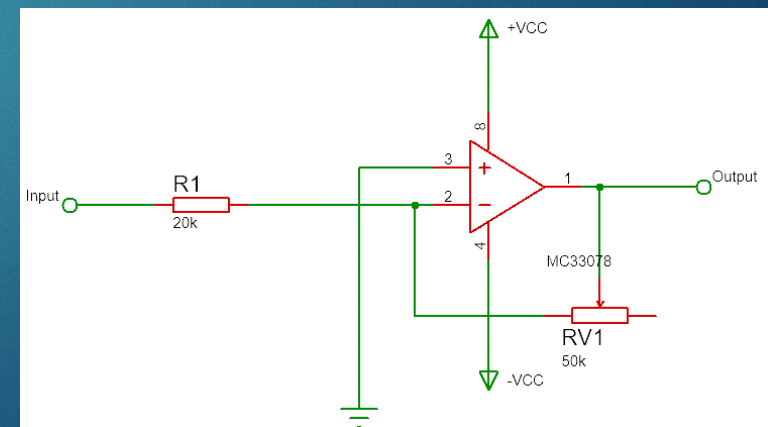
## ➤ o/p stage amp using MC33078:


- Used to adjust the required amplification .
- We use a variable gain amplifier.
- $G = -RV1/R1$ .
- RV1 is a variable resistor = 50k $\Omega$ .
- $R1 = 20k\Omega$  .




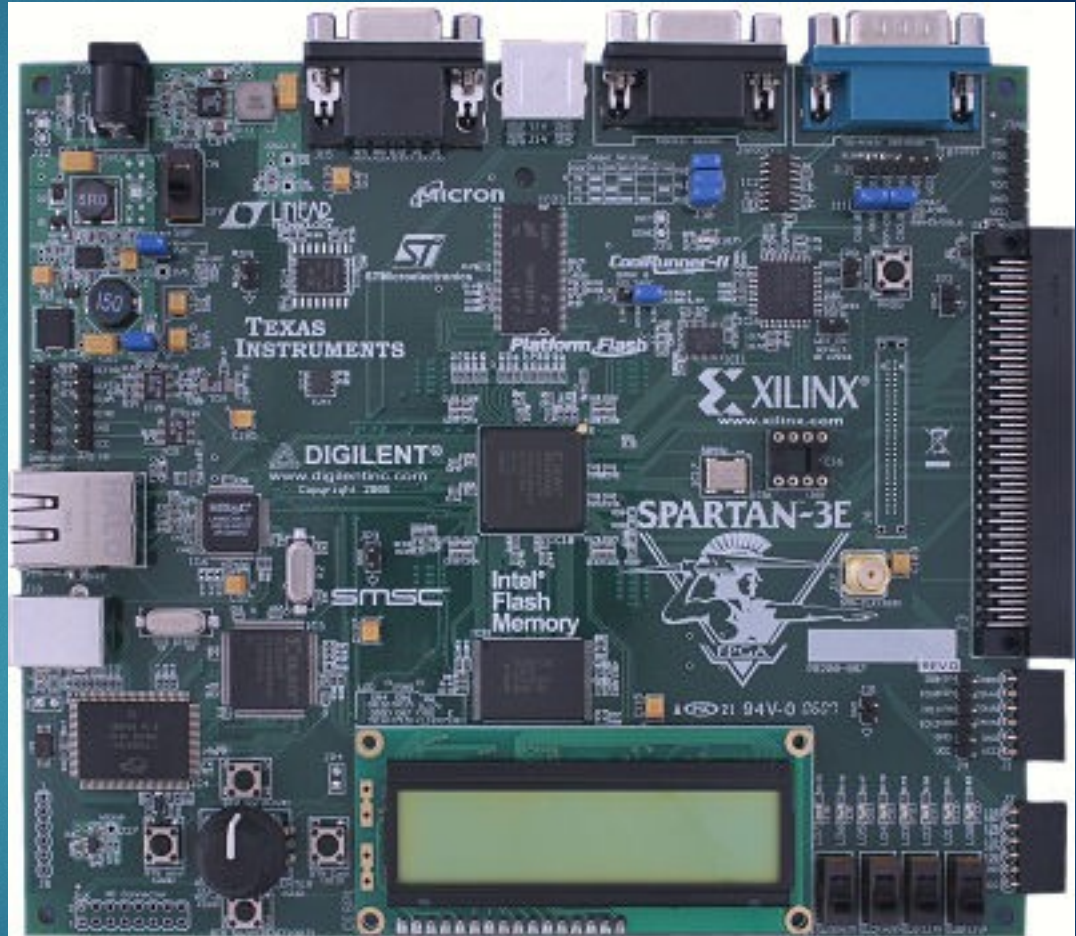
## ➤ Processing step using


- **FPGA** is the part which control when the gripper opened or closed.









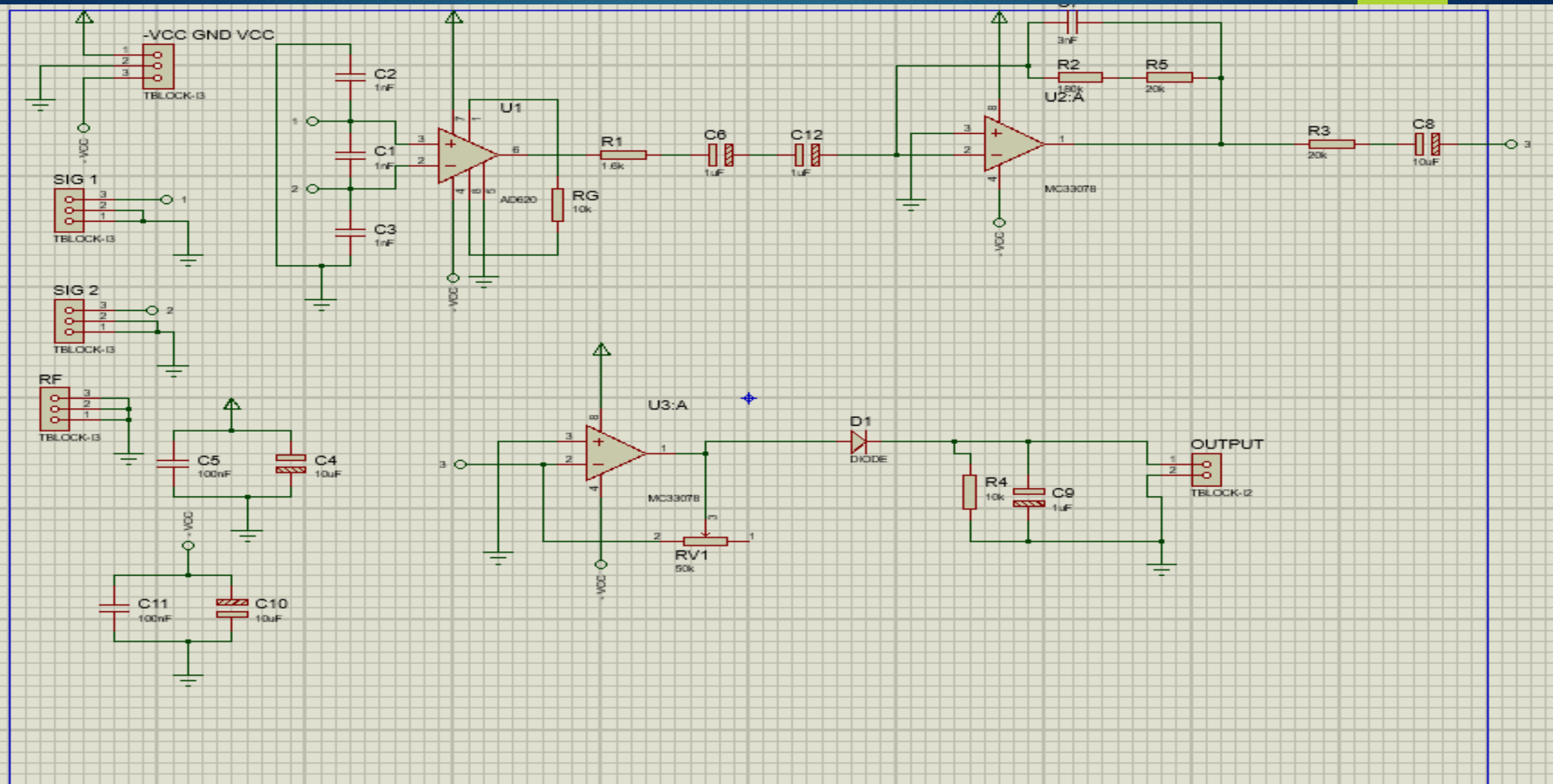
## ➤ Final Amplification and filtering schematic:








## ➤ PCB design:

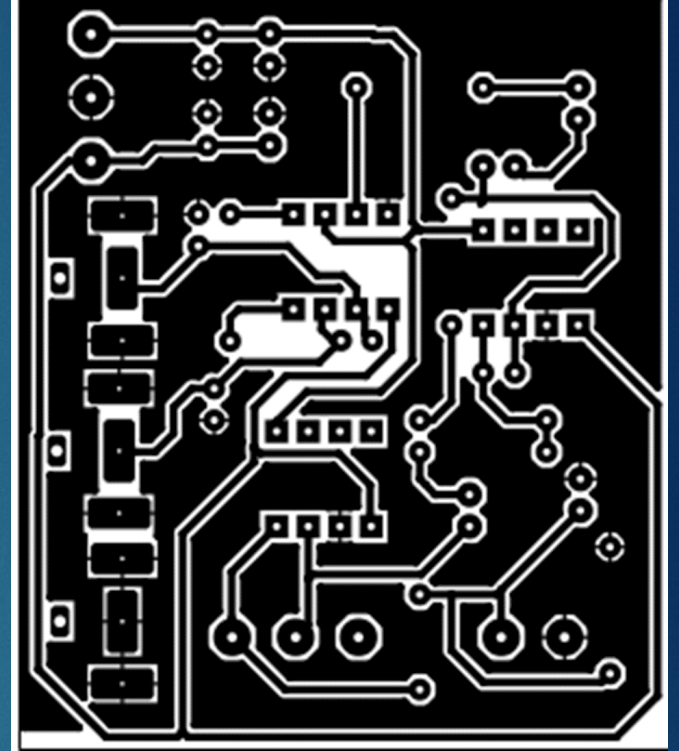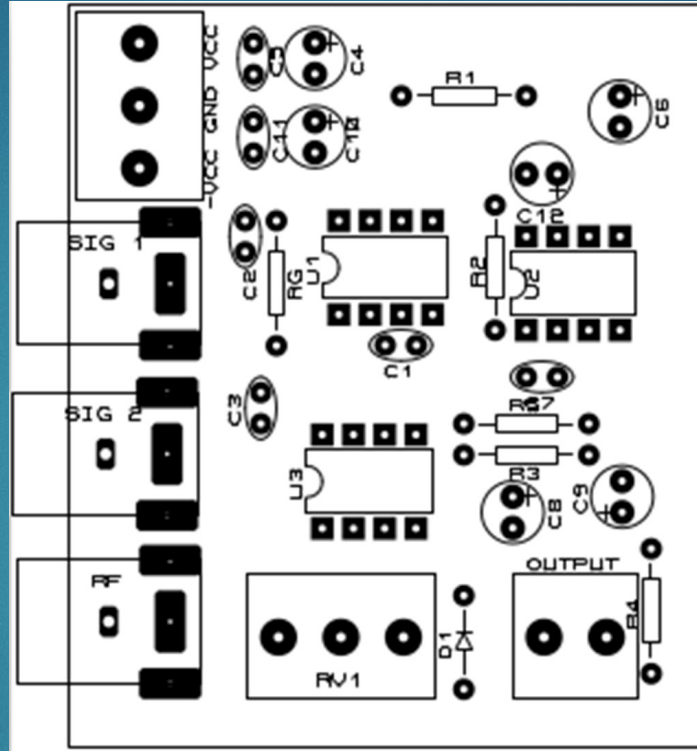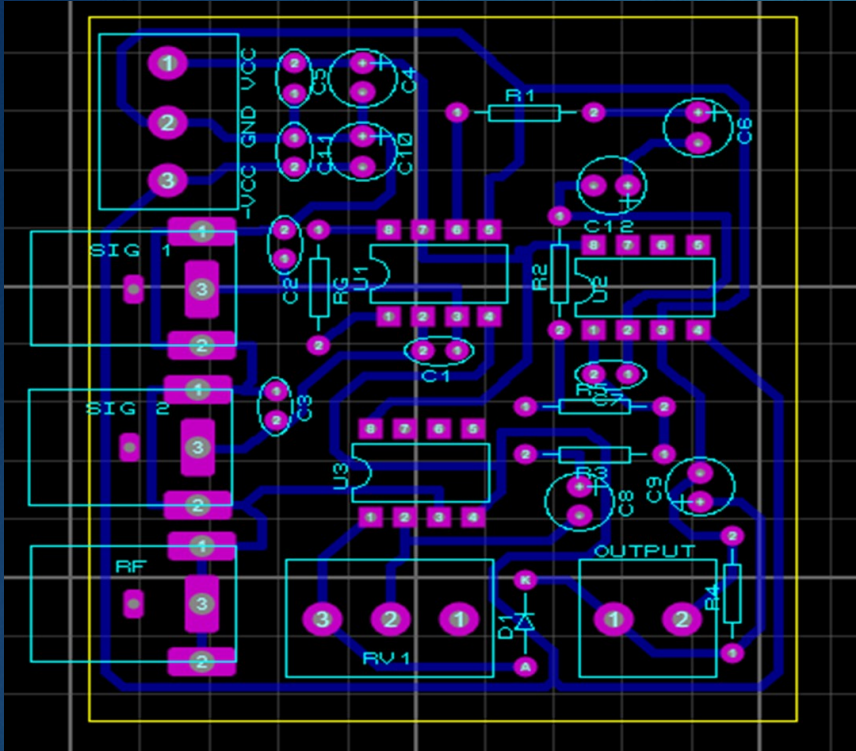




## ➤ Final PCB:

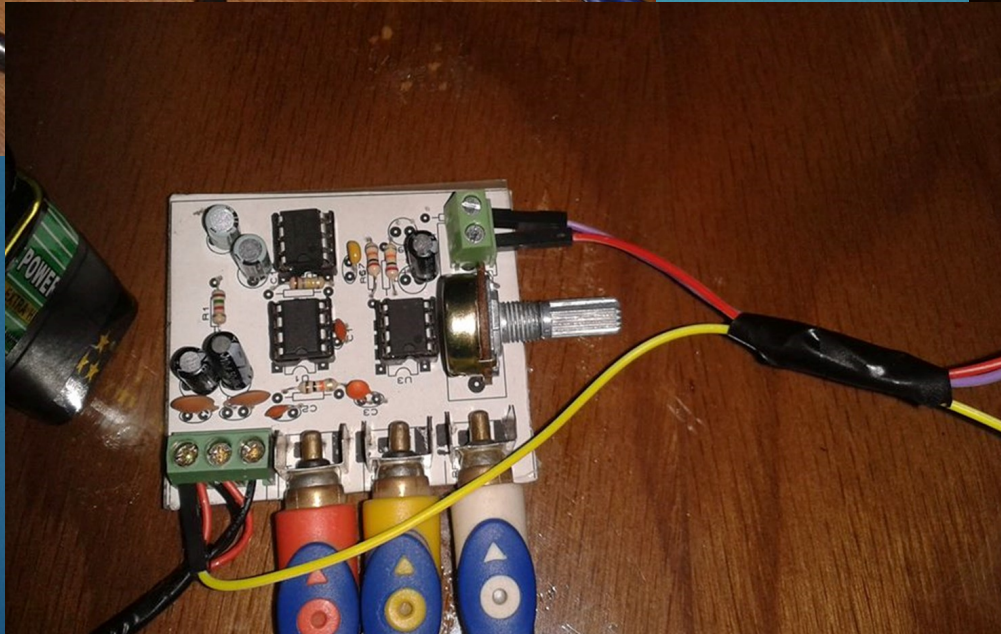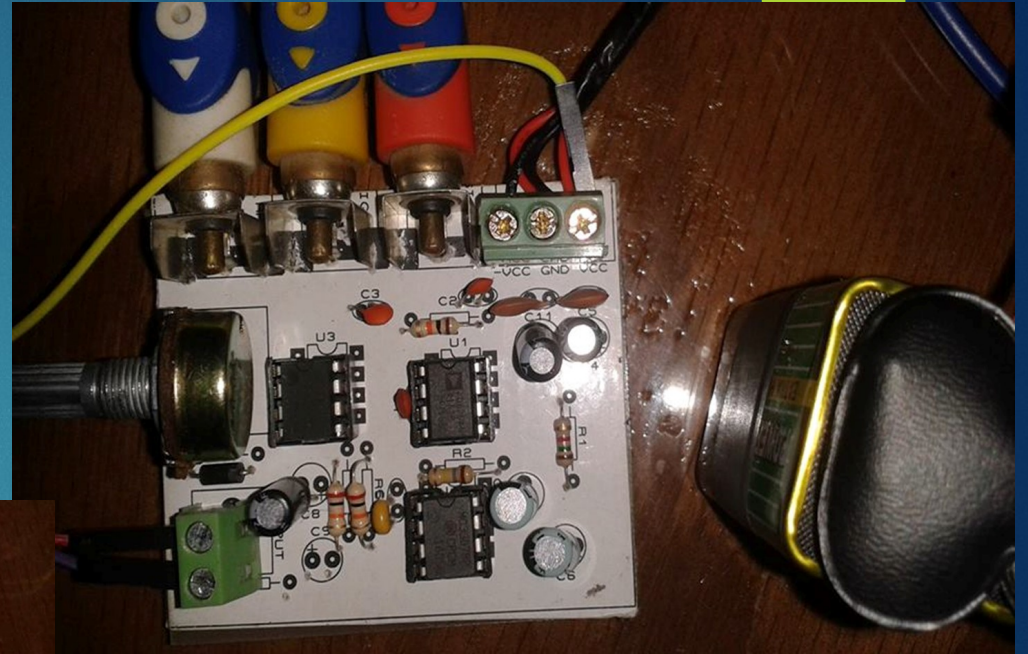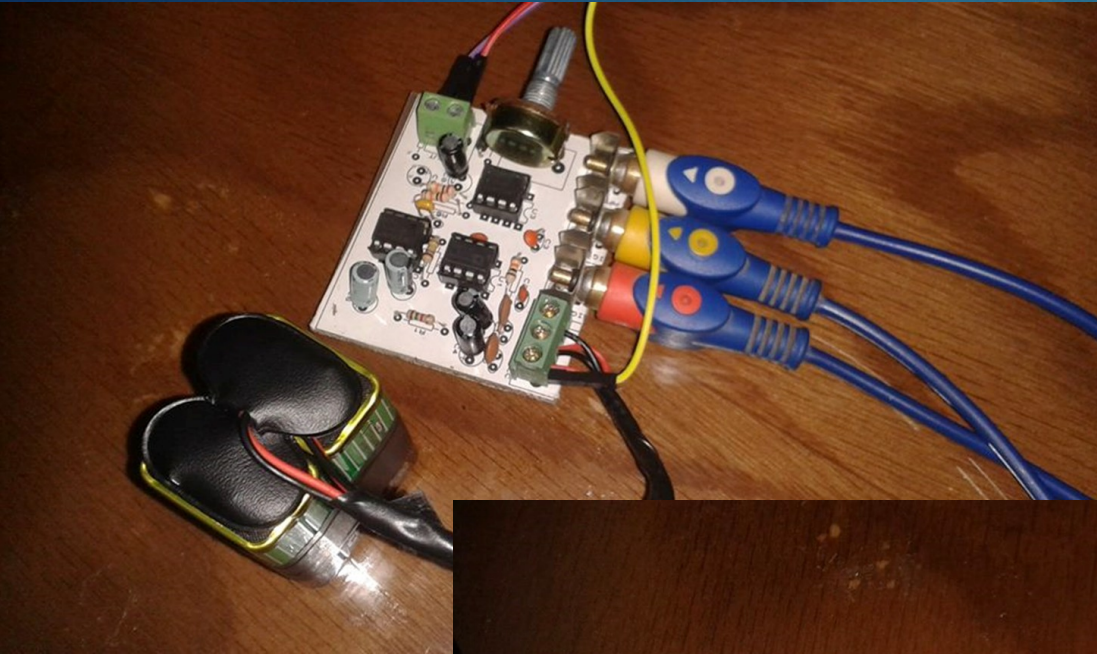



➤ Final signal:

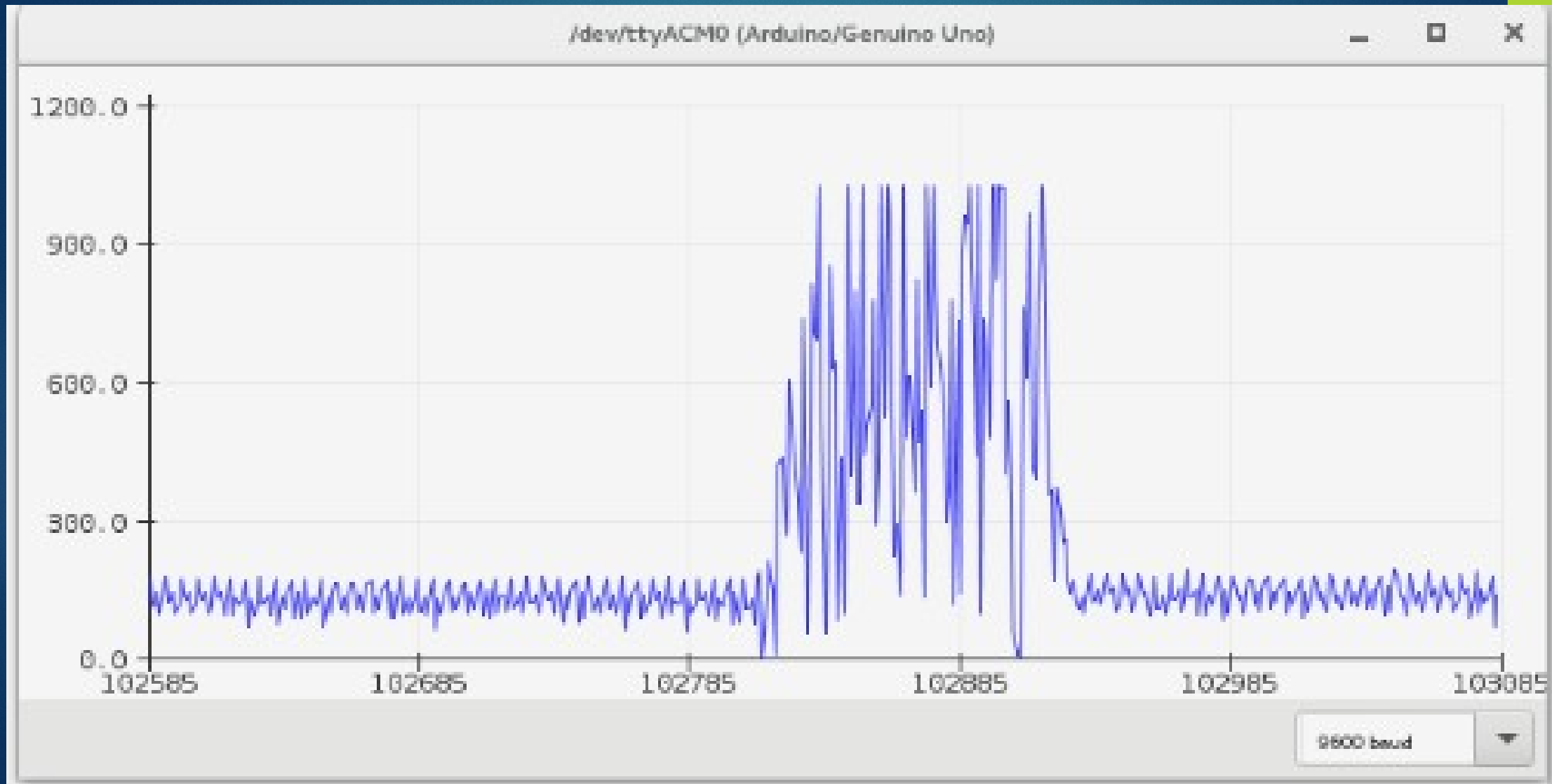

➤ Video:





